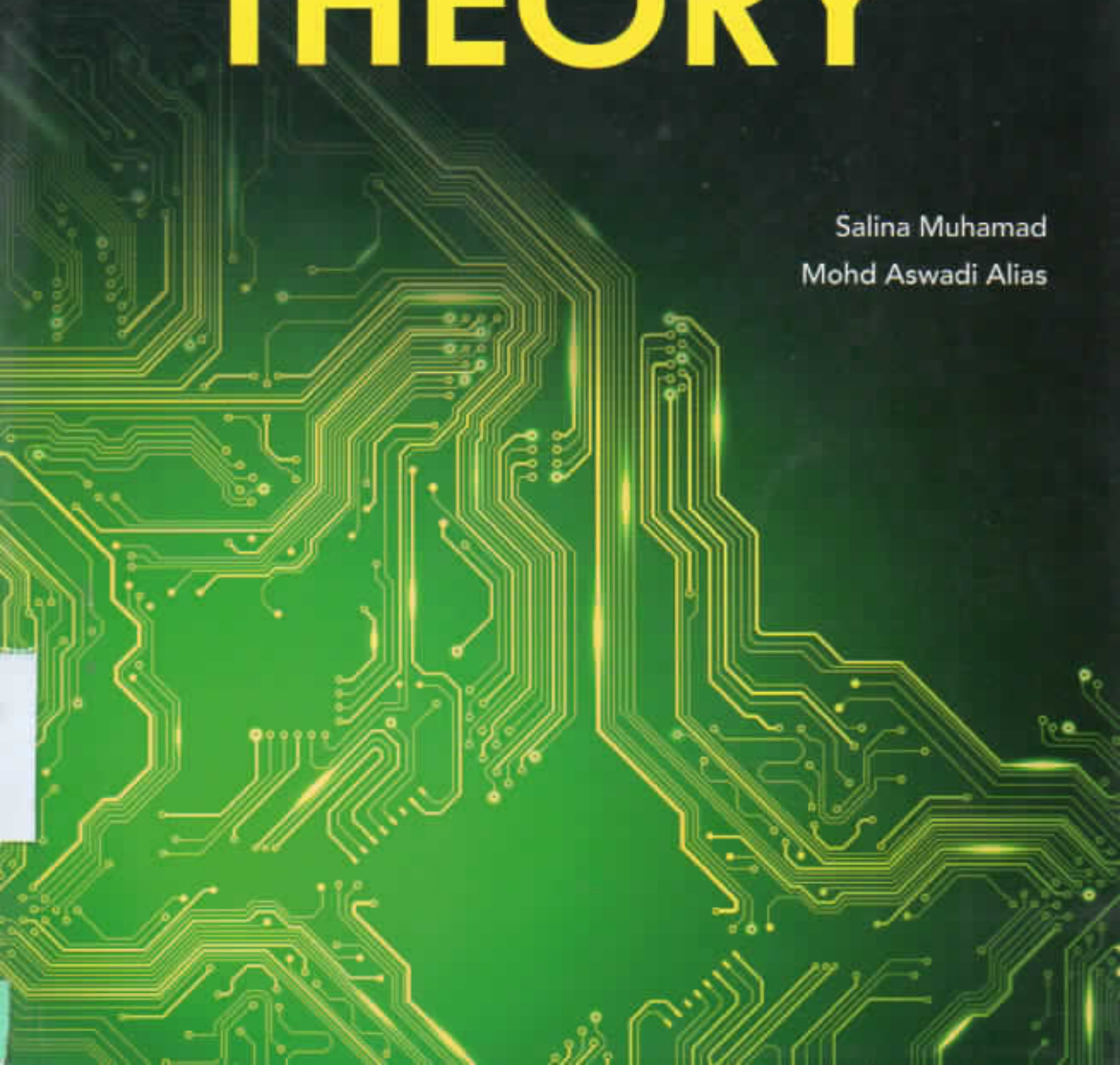



OXFORD

CIRCUIT THEORY

Salina Muhamad
Mohd Aswadi Alias



Sc
G21-815
M952
2018

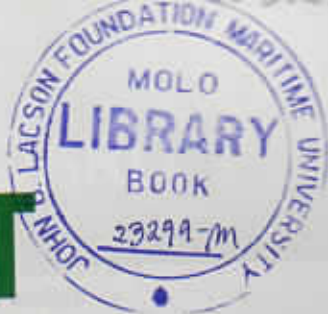

CIRCUIT THEORY

Salina Muhamad
Mohd Aswadi Alias

OXFORD
UNIVERSITY PRESS

CONTENTS

Oxford Advisory Board

Dedication

Preface

Acknowledgements

CHAPTER 1 Basic Concept

1.0	Introduction	2
1.1	The International System of Units	2
1.2	Charge, Current and Voltage	4
1.3	Power and Energy	8
1.4	Basic Circuit Elements	9
	<i>Summary</i>	13
	<i>Exercises</i>	13

CHAPTER 2 Basic Voltage and Current Laws

2.0	Introduction	16
2.1	Ohm's Law	16
2.2	Nodes, Branches, Paths and Loops	19
2.3	Series Resistors	21
2.4	Parallel Resistors	23
2.5	Series-Parallel Resistor	28
2.6	Kirchhoff's Laws	35
2.7	Voltage and Current Division	40
2.8	Delta-Wye and Wye-Delta Transformations	46
	<i>Summary</i>	51
	<i>Exercises</i>	52

CONTENTS

<i>Oxford Advisory Board</i>	iii
<i>Dedication</i>	v
<i>Preface</i>	vi
<i>Acknowledgements</i>	vii

CHAPTER 1 Basic Concept

1.0 Introduction	2
1.1 The International System of Units	2
1.2 Charge, Current and Voltage	4
1.3 Power and Energy	8
1.4 Basic Circuit Elements	9
<i>Summary</i>	13
<i>Exercises</i>	13

CHAPTER 2 Basic Voltage and Current Laws

2.0 Introduction	16
2.1 Ohm's Law	16
2.2 Nodes, Branches, Paths and Loops	19
2.3 Series Resistors	21
2.4 Parallel Resistors	23
2.5 Series-Parallel Resistor	28
2.6 Kirchhoff's Laws	35
2.7 Voltage and Current Division	40
2.8 Delta-Wye and Wye-Delta Transformations	46
<i>Summary</i>	51
<i>Exercises</i>	52

C H A P T E R 3 Systematic Analysis Methods

3.0	Introduction	58
3.1	Nodal Analysis	58
3.2	Mesh Analysis	74
3.3	Nodal Versus Mesh Analysis	86
	<i>Summary</i>	87
	<i>Exercises</i>	88

C H A P T E R 4 Circuit Theorems

4.0	Introduction	94
4.1	Superposition	94
4.2	Source Transformation	104
4.3	Thevenin's Theorem	111
4.4	Norton's Theorem	123
4.5	Maximum Power Transfer	130
	<i>Summary</i>	136
	<i>Exercises</i>	136

C H A P T E R 5 The Operational Amplifier

5.0	Introduction	142
5.1	Background of Op-Amp	142
5.2	Ideal Op-Amp	146
5.3	Selected Op-Amp Circuits	150
	<i>Summary</i>	161
	<i>Exercises</i>	161

CHAPTER 6 Capacitors and Inductors

6.0	Introduction	168
6.1	Capacitors	168
6.2	Inductors	174
6.3	Series-Parallel Connection	179
	<i>Summary</i>	190
	<i>Exercises</i>	190

CHAPTER 7 First Order Circuits

7.0	Introduction	194
7.1	Source-Free RC Circuit	194
7.2	Source-Free RL Circuit	201
7.3	Forced Response	206
7.4	Step-Response of RC and RL Circuits	208
	<i>Summary</i>	215
	<i>Exercises</i>	216

CHAPTER 8 Second Order Circuits

8.0	Introduction	222
8.1	Natural Response	222
8.2	Step Response	239
	<i>Summary</i>	245
	<i>Exercises</i>	245
	<i>Model Exam Paper 1</i>	249
	<i>Model Exam Paper 2</i>	250
	<i>References and Further Reading</i>	251
	<i>Index</i>	252

INDEX

A

Atoms, 5

B

Basic circuit elements, 9
 passive elements, 9
 active elements, 9,12
Basic concept, 1,16,19
Basic voltage, 15
Bohr model, 5
Branches, 19,20

C

Capacitors, 168–174,179–185
Capacitor behaviour, 171
 electric field, 9,170–172
Capacitor characteristics, 169–170
 capacitance (C), 170
 leakage current, 170
 polarization, 171
 tolerance, 10,11,170
 working temperature (T), 171
 working voltage, 170
Charge, 5
Circuit theorems, 94
 maximum power transfer, 130–135
 Norton's theorem, 123
 source transformation, 104–110,123
 superposition, 94–95,98,101
 Thevenin's theorem, 111–123
Cramer's rule, 61
Current, 5–7
Current division, 40,43
Current laws, 15

D

Delta-wye transformation, 47,48
Difference amplifier, 157–159

E

Electrical quantities, 2,4
 symbols, 2–4,11–12,168,174
 units, 2–4,9
Electrons, 5–6,94,169
Energy, 8–9

F

First order circuits, 193
 natural response, 194–195,201–202,
 206,222,227–228,234
 RC circuits, 194,206
 RL circuits, 208
 step response, 208–215
Forced response, 206,208

I

Ideal op-amp, 142–143,146
 difference amplifier, 157–159
 inverting voltage amplifier, 150,151
 non-inverting voltage amplifier, 152
 summing amplifier, 154–157
Inductors, 174–179,185–189
 energy storage, 174,206,222,225,233
 fixed, 10,14,130,175
 magnetic field, 174–175,177–178
 variable, 174–175
Inductor behaviour, 175
 electromotive field, 177
 magnetic field, 174–175,177–178
Inductor characteristics, 177
 DC resistance (DCR), 176
 inductance (L), 175
 rated current, 177
 saturation current, 176–177
 self-resonant frequency, 177
 winding self-capacitance, 177
International System of Units (SI), 2–4
Inverting voltage amplifier, 150–151
 current-to-voltage converter, 150

K

- Kirchhoff's laws, 35–40
- Kirchhoff's Current Law (KCL), 35
- Kirchhoff's Voltage Law (KVL), 36

L

- Loop analysis, 74
- Loops, 19–21

M

- Matrix form, 61–65, 74–75
- Maximum power transfer, 94, 130–135
- Maximum power transfer theorem, 130
- Maxwell's circulating currents method, 74
- Mesh analysis, 74–87
 - dependent source, 67, 81

N

- Natural response, 194–195, 201–202, 206, 222, 227–228, 234
- Nodal analysis, 58, 60–61, 64, 67, 70, 72, 74–75, 78, 81, 86–87, 203
 - dependent source, 12, 67, 81, 102, 104, 110, 120–121, 124, 126–127, 194, 222
 - independent nodal equations, 58
 - independent source, 12, 67, 120–121, 126, 194, 222
 - nodal equations, 58, 87
 - nodal voltages, 58
 - reference node, 7, 41, 58–61, 64, 67, 69–71, 73, 144
- Nodal versus mesh analysis, 86
- Nodes, 7, 19–20, 29–32, 37, 58–61, 64, 67, 69–71, 73, 87, 104, 149
- Non-inverting voltage amplifier, 152
 - positive voltage gain, 152
- Non-reference node, 71, 73
- Norton's theorem, 94, 123–124

O

- Ohm's law, 16, 22–23, 26–28, 31, 35–36, 39, 43–46, 58, 96, 104
- Ohm's law triangle, 16
- Operational amplifier (op-amp), 142

- amplification, 150
 - ideal op-amp, 142–143, 146
 - mathematical operations, 142, 150, 154
 - model, 5, 9, 142, 145–146, 208
 - non-ideal op-amp, 141
 - selected (op-amp) circuits, 150

P

- Parallel resistors, 16, 23–26, 28, 32–33, 187
- Parallel RLC circuit, 222–223, 225, 234, 238–239, 242–243
 - critically-damped case, 228, 234, 240, 242
 - overdamped case, 228, 234, 240, 242
 - underdamped case, 228, 234, 240, 243
- Paths, 19, 24, 44
- Power, 8–9
 - absorbing, 8–9, 40
 - supplying, 9
- Power supply, 143
- Protons, 5

R

- Reference node, 7, 58–61, 64, 67, 69–71
- Resistor, 9–12
 - fixed, 10
 - variable, 10

S

- Second order circuits, 222
 - natural response, 222, 227–228, 234
 - parallel RLC circuits, 222
 - serial RLC circuits, 222
 - step response, 222, 239
- Serial RLC circuit, 222, 239
 - critically-damped case, 240, 242
 - overdamped case, 240, 242
 - underdamped case, 240, 243
- Series, 21–22, 24, 28–36, 179–183, 185–186, 225, 239
- Series resistors, 21–22, 29, 180
- Series-parallel connection, 179
 - capacitors in parallel circuits, 179
 - capacitors in series circuits, 181
 - capacitors in series and parallel circuits, 183
 - inductors in parallel circuits, 186
 - inductors in series circuits, 185

- inductors in series and parallel circuits, 188
- Series-parallel resistor, 28
- SI Units, 2-4
- Source-free *RC* circuits, 194
- Source-free *RL* circuits, 201
- Source transformation, 104-110
- Step-response of *RC* and *RL* circuits, 208
 - series *RLC* circuit, 239
- Summing amplifier, 154-157
- Supermesh, 83-87
 - mesh currents, 79,84-85
 - meshes, 100
 - loops, 19-21,37,74-76,79,83-85
- Supernode, 70-71,73,85-86
 - non-reference nodes, 71
- Superposition, 94-103
 - analysis, 95,97-98
 - parallel analysis, 95
 - series analysis, 95
- Systematic analysis methods, 57
 - mesh analysis, 74-86
 - nodal analysis, 58-73

T

- Thevenin equivalent circuit, 111-120
- Thevenin resistance, 111
- Thevenin voltage source, 111
- Thevenin's theorem, 111

V

- Variable, 222
- Voltage, 7-8,40,150,152
- Voltage division, 40
- Voltage divider, 40-43

W

- Wheatstone Bridge circuit, 78
- Wye-delta transformation, 46-47,49

